

EE3301

ANALOG ELECTRONICS

Gayathri Thilakarathne

Department of Electrical and Information Engineering.

Email: gayathrit@eie.ruh.ac.lk

Filters

Time Domain Signals

Basic Characteristics

- Peak Amplitude
- Period (time)
- Frequency
- Phase
- Wavelength

Measured using:
Oscilloscope

Frequency Domain Signals

Basic Characteristics

- Peak Amplitude
- Frequency

Measured using:
Spectrum Analyzer

A Time Domain (TD) waveform is a waveform (signal) that has a variation in *time*.

Example:

In a sine wave,

$$e(t) = A \sin(\omega t) = A \sin(2\pi f t)$$

Where;


A – amplitude (V)

ω – angular (circular) frequency (rad)

f – frequency (Hz)

t –time

•

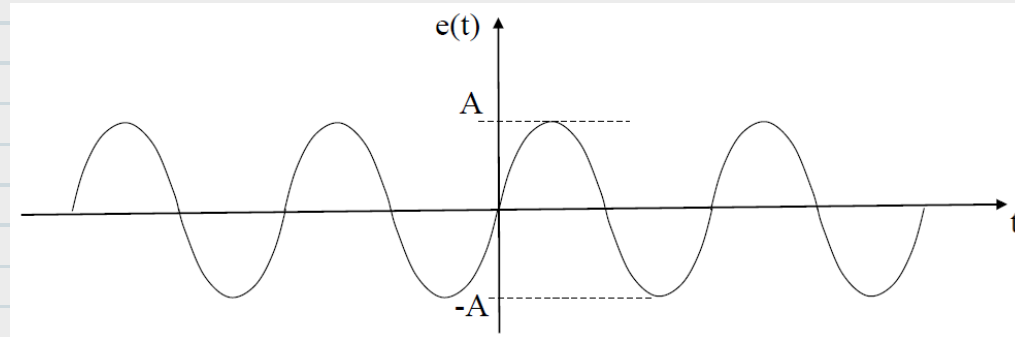


A sine wave can also have a phase angle ϕ ,

Then;

$$e(t) = A \sin(\omega t + \phi) = A \sin(2\pi f t + \phi)$$

T in Figure represent the time corresponding to phase angle ϕ .

o

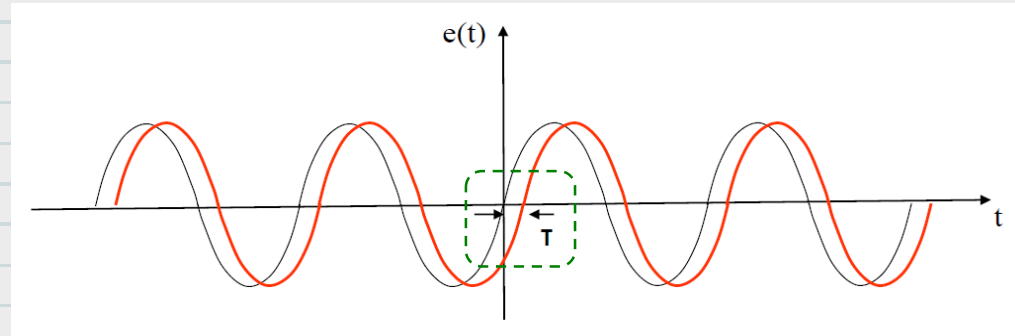

Time Domain \longrightarrow Frequency Domain

- Fourier Transform
- Laplace Transform
- Z – transform

*** *These are covered in Signals and Systems.*

o

o

What is a filter?

A device that allows signals having frequencies in a certain range called *passband* to *pass* through *while attenuating all other frequencies*.





o

o

What is a filter?

A device that allows signals having frequencies in a certain range called *passband* to *pass* through *while attenuating all other frequencies*.

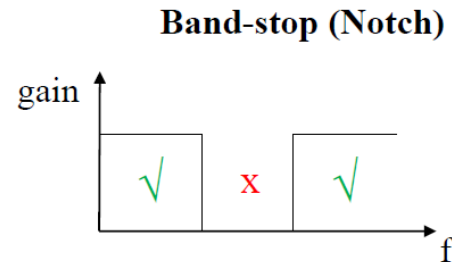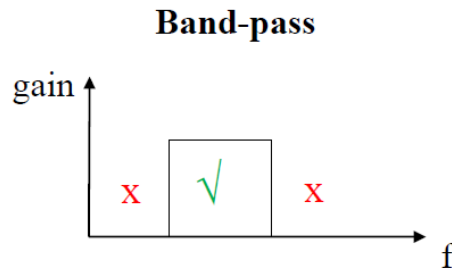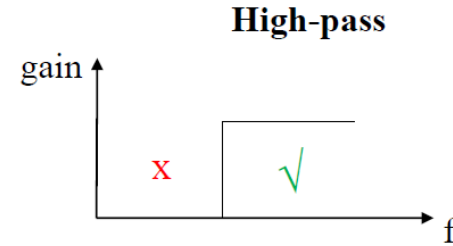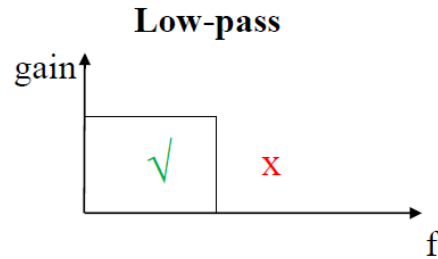
A **Ideal** filters, (sometimes) called as *brick wall* filters.




An *ideal filter* has *identical gain at all frequencies* in its pass band and *zero gain at all frequencies outside* of its passband.

But in practical filters;


High Pass Filter

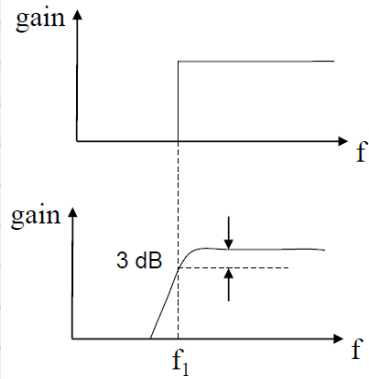


Low Pass Filter

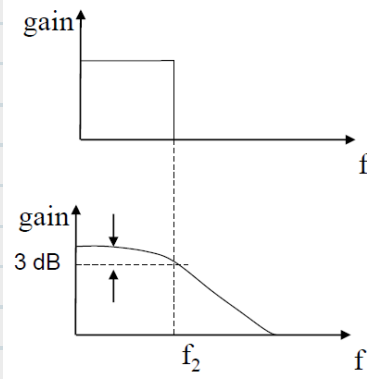


Band Pass Filter

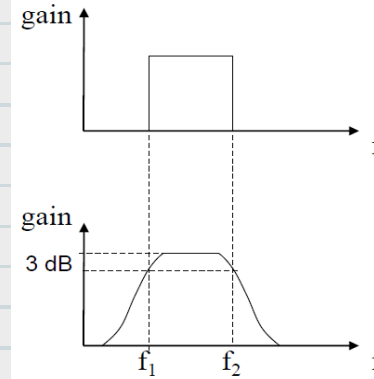


Band Stop Filter

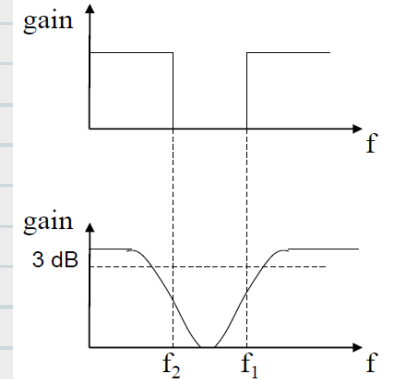

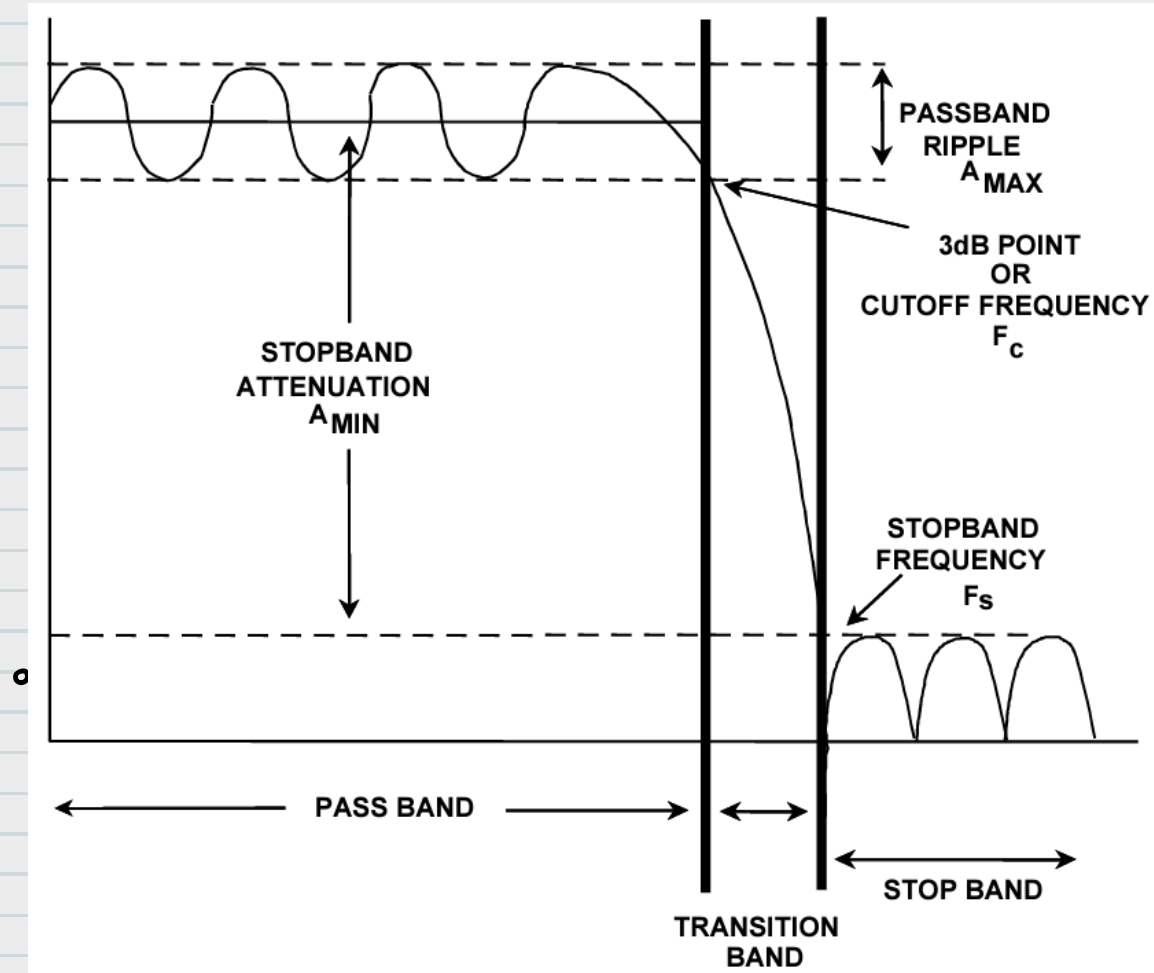f_1 and f_2 are cut-off frequencies at which the response is down 3 dB from its maximum value in the passband.



Filter Classification

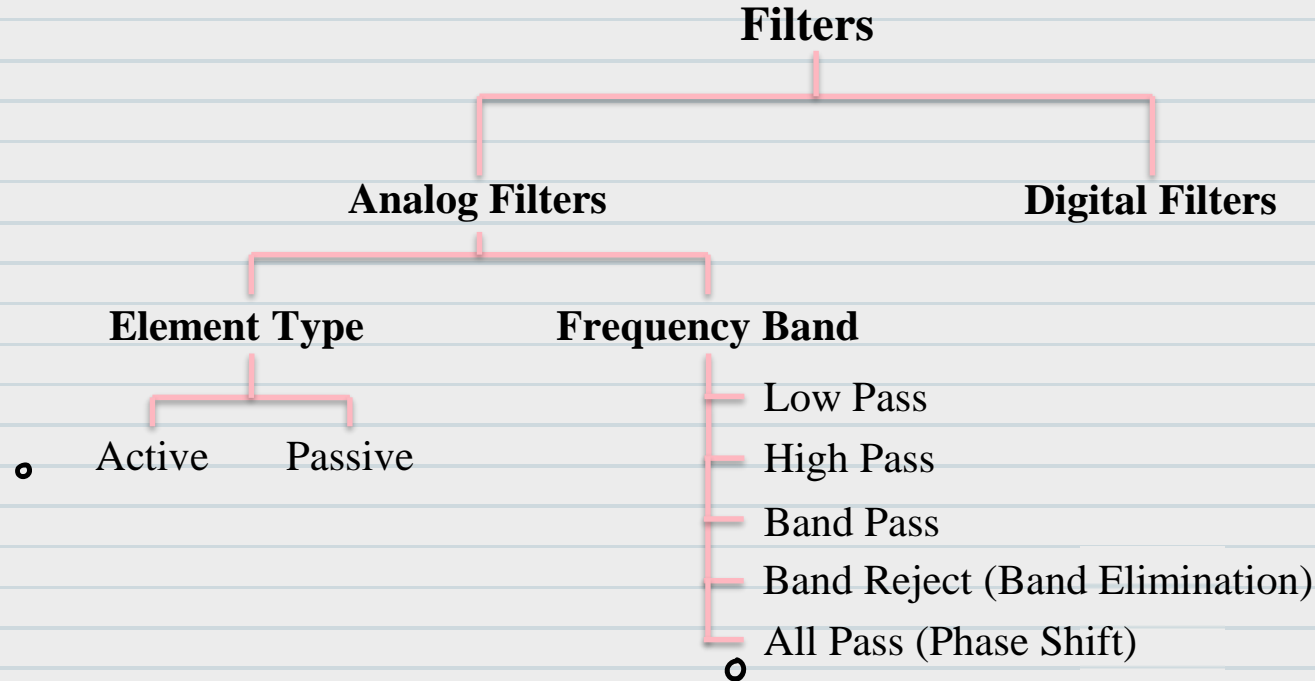

Types of Filters

1. Passive Filters

- Designed with passive components.

Examples:

Capacitors, Resistors, Inductors

2. Active Filters

- Designed with active components.

Examples:

Transistors, op-amps and RC networks

- — **Needs external DC supply

1. Passive Filters

- Contains only **R**, **L**, and **C** components (*not* necessary that *all three* be present).
- L is often omitted (on purpose) from passive filter designs.

Because,

- The size and cost
- Adds an internal resistance to the which cannot be ignored

- Q is the *quality factor* of the filter. Sometimes given as α .

Where;

$$\alpha = \frac{1}{Q}$$


- The higher the Q;
 - Better the filter
 - Lower the losses
 - Closer to being perfect filter

$$Q = 2\pi \times \frac{\text{Energy stored}}{\text{Energy dissipated per cycle}}$$

- Filters are classified by their **order** (an integer number), also called the **number of poles** (*a resistor + Capacitor pair*).
 - The order here refers to the order of the **polynomial(s)** that are used to define the filter.
- Higher the order of a filter;
 - Response will be closer to the ideal case
 - More complex the circuitry

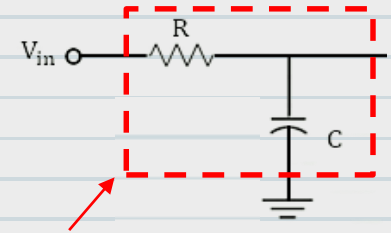*****Means an *Ideal filter*, can be approached by making the **order** of the filter **higher and higher**.**

- Frequency response outside the passband of a filter of order **n** has a slope of **$20n$ dB/decade** or **$6n$ dB/octave**.



First order or single pole

Roll – off Rate

The slope of the transition region of a response curve;

$$\text{Roll – off rate} = \frac{\text{gain (dB)}}{\text{frequency (decade)}}$$

****Magnitude changes 20 dB when frequency changes tenfold or one decade.**

The # of poles determine the roll – off rate of a filter.


Example:

The roll – off rate of


$n = 1$; a first order (or single-pole) filter = -20 dB/decade

$n = 2$; a second order (or two-pole) filter
= $-20 \text{ dB/decade} \times 2 = -40 \text{ dB/decade}$

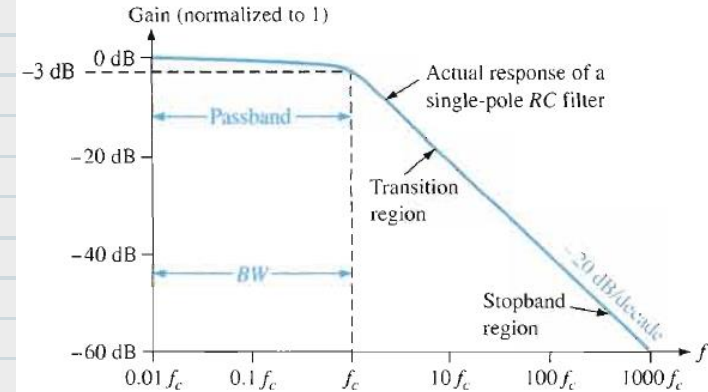$n = 3$; a third order (or three-pole) filter
= $-20 \text{ dB/decade} \times 3 = -60 \text{ dB/decade}$



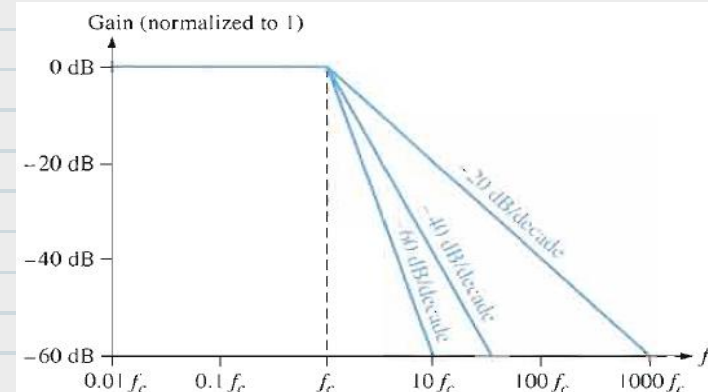Response curve of a first Order (Single pole) low pass filter



Response curves for several order (several pole) low pass filters

Voltage Transfer Function in the frequency domain

- The main parameter in a filter.

$$H(j\omega) = \frac{V_O}{V_{in}}$$

Where;

V_O – Output Voltage

V_{in} – Input Voltage

- $H(j\omega)$ is a complex number, so it has both the *magnitude* and the *phase*.
- Filters in general, introduce a *phase difference* between *input* and *output* signals.

General first – order low pass filters

- In general, the voltage transfer function of a first-order low – pass filter is in the form:

$$H(j\omega) = \frac{K}{1 + j\frac{\omega}{\omega_c}}$$

Where;

$$|H(j\omega)|_{\max} = |K|$$

K – A scaling factor chosen by the designer to give a specific gain.

Magnitude:

$$|H(j\omega)| = \frac{|K|}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

Phase:

$$\angle H(j\omega) = -\frac{|K|}{K} \tan^{-1}\left(\frac{\omega}{\omega_c}\right)$$

Where;

ω_c – The cut – off frequency

RC Low pass filter

A series RC circuit act as a low pass filter.

When *no load* resistance R_L , (called as *open-loop transfer function*);

V_o can be found from the voltage divider formula;

$$V_o = \left(\frac{X_C}{X_C + R} \right) V_{in}$$

Where;

V_o – Output voltage


V_{in} – Input voltage

X_C – Capacitive Reactance

$$X_C = \frac{1}{j\omega C}$$

☒ Impedance

☐ Resistance

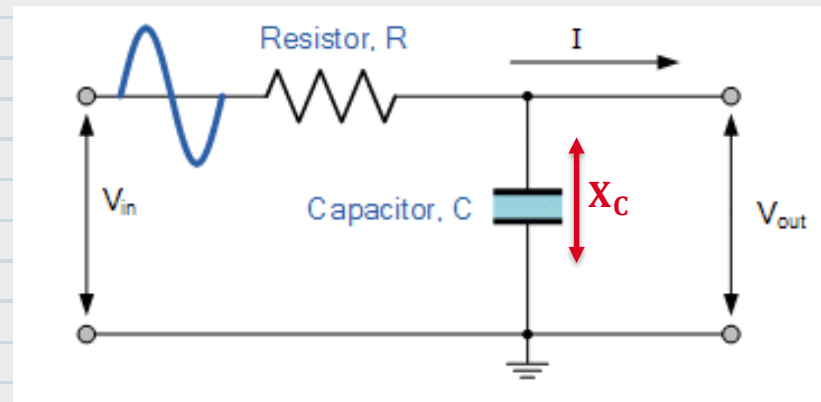

RC Low pass filter

A series RC circuit act as a low pass filter.


When *no load* resistance R_L , (called as *open-loop transfer function*);

V_o can be found from the voltage divider formula;

$$V_o = \left(\frac{X_C}{X_C + R} \right) V_{in}$$

$$V_o = \left(\frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \right) V_{in}$$
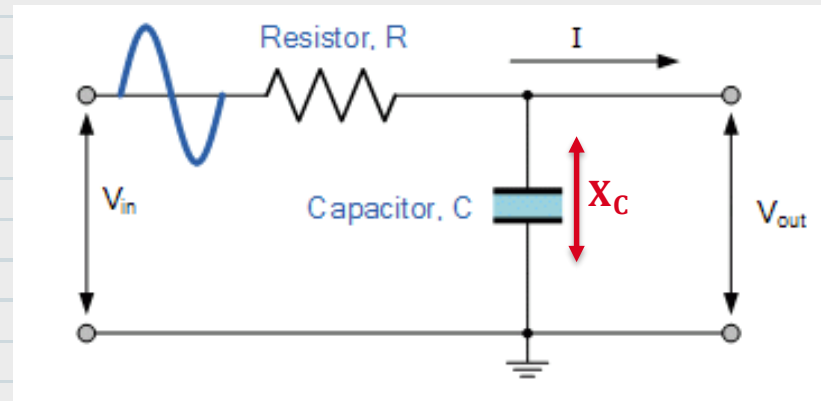
$$H(j\omega) = \frac{V_o}{V_{in}} = \left(\frac{1}{1 + j\omega CR} \right)$$



If we consider the voltage transfer function of a first-order low-pass filter;

$$H(j\omega) = \left(\frac{\mathbf{1}}{\mathbf{1} + j\omega\mathbf{RC}} \right) \quad \text{similar to} \quad H(j\omega) = \frac{\mathbf{K}}{1 + j\frac{\omega}{\omega_c}}$$

Means;

$$\mathbf{K} = \mathbf{1} \quad \text{and} \quad \omega_c = \frac{1}{RC}$$

The input impedance Z_i ;

$$Z_i = R + \frac{1}{j\omega C} \quad \text{and} \quad Z_i|_{\min} = R$$

•

The output impedance Z_o ;

$$Z_o = R \parallel \frac{1}{j\omega C} \quad \text{and} \quad Z_o|_{\max} = R$$

•

RL Low pass filter

A series RL circuit act as a low pass filter.

V_o can be found from the voltage divider formula;

$$V_o = \left(\frac{R}{X_L + R} \right) V_{in}$$

Where;

X_L – Inductive Reactance


$$X_L = j\omega L$$

☒ Impedance

☐ Resistance

$$V_o = \left(\frac{R}{j\omega L + R} \right) V_{in}$$
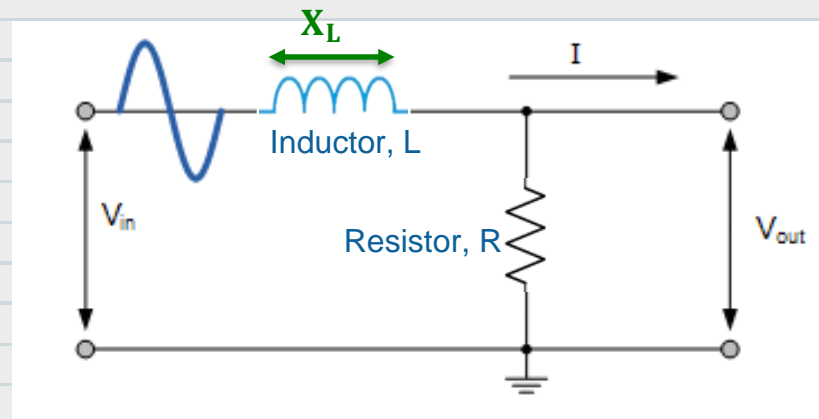
$$H(j\omega) = \frac{V_o}{V_{in}} = \left(\frac{1}{1 + \frac{j\omega L}{R}} \right)$$



If we consider the voltage transfer function of a first-order low-pass filter;

$$H(j\omega) = \left(\frac{\mathbf{1}}{1 + j\omega \frac{\mathbf{L}}{\mathbf{R}}} \right) \quad \text{similar to} \quad H(j\omega) = \frac{\mathbf{K}}{1 + j \frac{\omega}{\omega_c}}$$

Means;

$$\mathbf{K} = \mathbf{1} \quad \text{and} \quad \omega_c = \frac{\mathbf{R}}{\mathbf{L}}$$

o

o

General first – order high pass filters

- In general, the voltage transfer function of a first-order high – pass filter is in the form:

$$H(j\omega) = \frac{K}{1 - j \frac{\omega_c}{\omega}}$$

Where;

ω_c – The cut – off frequency of the filter

- Called as a high pass filter because $|H(j\omega)| = 0$ for $\omega = 0$ and $|H(j\omega)|$ is a constant for high frequencies.

RC High pass filter

The open-loop voltage transfer function of this filter is:


$$H(j\omega) = \frac{V_o}{V_{in}} = \left(\frac{R}{X_C + R} \right) \quad \text{Where; } X_C = \frac{1}{j\omega C}$$

$$H(j\omega) = \frac{V_o}{V_{in}} = \left(\frac{1}{1 + \frac{1}{j\omega CR}} \right) = \left(\frac{1}{1 - j\left(\frac{1}{\omega CR}\right)} \right)$$

If we consider the voltage transfer function of a first-order high – pass filter;

Where;
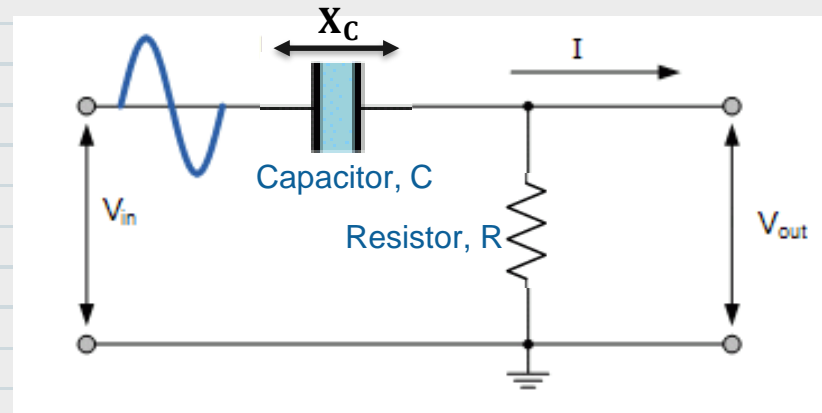
$$K = 1 \quad \text{and} \quad \omega_c = \frac{1}{RC}$$



Similarly;

The input impedance Z_i ;

$$Z_i = R + \frac{1}{j\omega C} \quad \text{and} \quad Z_{i|\min} = R$$

The output impedance Z_o ;

$$Z_o = R \parallel \frac{1}{j\omega C} \quad \text{and} \quad Z_{o|\max} = R$$

RL High pass filter

The open-loop voltage transfer function of this filter is:


$$H(j\omega) = \frac{V_o}{V_{in}} = \left(\frac{X_L}{X_L + R} \right)$$

Where; $X_C = j\omega L$

$$H(j\omega) = \frac{V_o}{V_{in}} = \left(\frac{1}{1 + \frac{R}{j\omega L}} \right) = \left(\frac{1}{1 - j\left(\frac{R}{\omega L}\right)} \right)$$

Where;

$$\omega_c = \frac{R}{L}$$

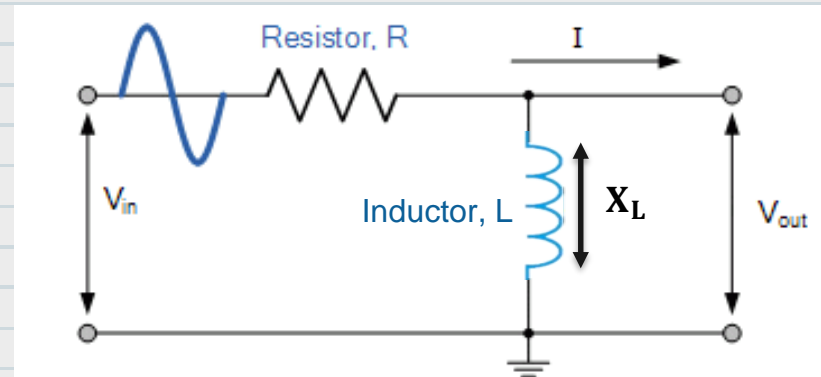

Similarly;

The input impedance Z_i ;

$$Z_i = R + j\omega L \quad \text{and} \quad Z_i|_{\min} = R$$

The output impedance Z_o ;

$$Z_o = R \parallel j\omega L \quad \text{and} \quad Z_o|_{\max} = R$$

Band Pass Filters

A band pass filter allows signals with a *range of frequencies* (*passband*) to pass through and attenuates signals with frequencies outside this range.

$$\text{Centre Frequency, } \omega_o = \sqrt{\omega_l \omega_u}$$

$$\text{Bandwidth, } BW = \omega_u - \omega_l$$



$$\text{Quality Factor, } Q = \frac{\omega_o}{BW}$$

Where;

ω_l – The lower cut – off frequency

ω_u – The upper cut – off frequency

ω_o – The centre frequency

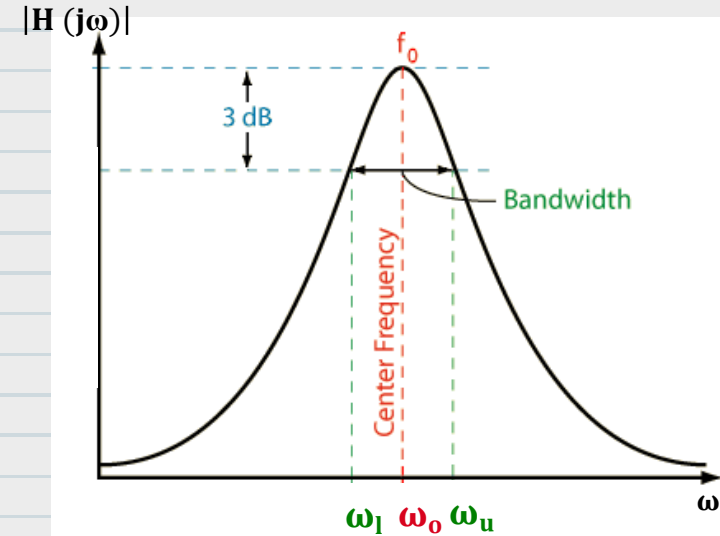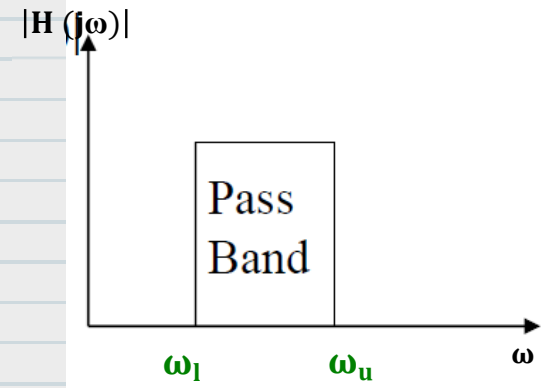

1**2**

Band Pass Filter = High Pass Filter + Low Pass Filter

- Band Pass filters are *Second-order filters*.
Second-order band pass filters include two storage elements.
(two capacitors, two inductors, or one of each).
- The transfer function for a second-order band-pass filter can be written as;

$$H(j\omega) = \frac{K}{1 + jQ\left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega}\right)}$$

Magnitude:

$$|H(j\omega)| = \frac{|K|}{\sqrt{1 + Q^2\left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega}\right)^2}}$$

Phase:

$$\angle H(j\omega) = -\frac{|K|}{K} \tan^{-1}\left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega}\right)$$


- The maximum value of $|H(j\omega)|_{\max} = |K|$ is the filter gain.
- The lower and upper cut-off frequencies can be calculated by noting that;
The cutoff frequency is defined as the frequency where the amplitude of $H(j\omega)$ is $\frac{1}{\sqrt{2}}$ times the DC amplitude (approximately -3dB, half power point).
- $|H(j\omega)|_{\max} = |K|$, setting $|H(j\omega_c)| = \frac{|K|}{\sqrt{2}}$ and solving for ω_c ;

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} |H(j\omega)|_{\max} = \frac{|K|}{\sqrt{2}} = \frac{|K|}{\sqrt{1 + Q^2 \left(\frac{\omega_c}{\omega_o} - \frac{\omega_o}{\omega_c} \right)^2}}$$

$$\frac{|K|}{\sqrt{2}} = \frac{|K|}{\sqrt{1 + Q^2 \left(\frac{\omega_c}{\omega_o} - \frac{\omega_o}{\omega_c} \right)^2}}$$

o
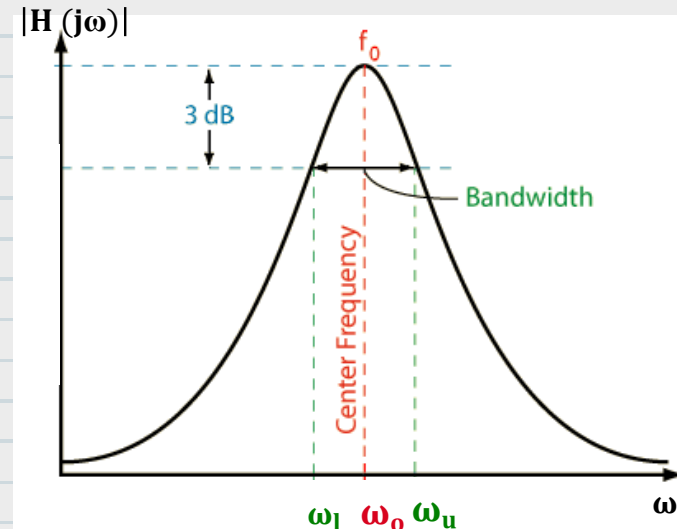
$$\omega_c = \omega_l \text{ Or } \omega_u$$



$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} |H(j\omega)|_{\max} = \frac{|K|}{\sqrt{2}} = \frac{|K|}{\sqrt{1 + Q^2 \left(\frac{\omega_c}{\omega_o} - \frac{\omega_o}{\omega_c} \right)^2}}$$


$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + Q^2 \left(\frac{\omega_c}{\omega_o} - \frac{\omega_o}{\omega_c} \right)^2}}$$

$$1 + Q^2 \left(\frac{\omega_c}{\omega_o} - \frac{\omega_o}{\omega_c} \right)^2 = 2$$

$$(\omega_c^2 - \omega_o^2)^2 = \frac{(\omega_o \cdot \omega_c)^2}{Q^2}$$

$$\omega_c^2 - \omega_o^2 \pm \left(\frac{\omega_o \cdot \omega_c}{Q} \right) = 0$$

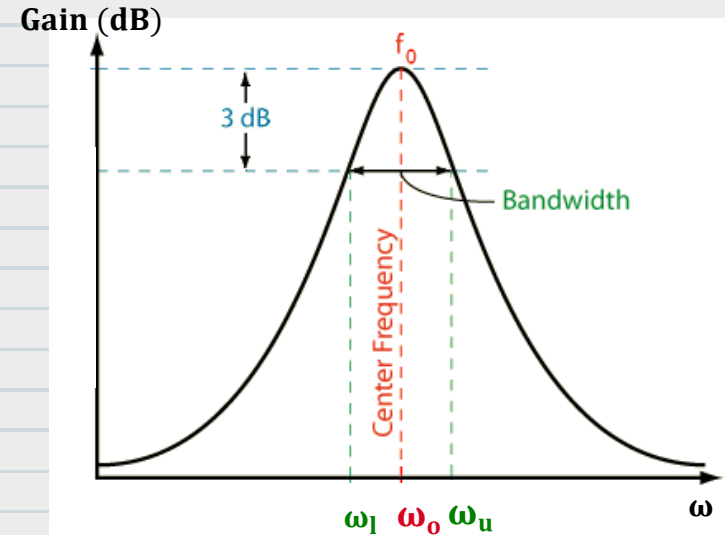This procedure will give two roots of ω_c : ω_l and ω_u .



$$\omega_c^2 - \omega_o^2 \pm \left(\frac{\omega_o \cdot \omega_c}{Q} \right) = 0$$

- This equation is really two quadratic equations.

$$\omega_c^2 - \omega_o^2 + \left(\frac{\omega_o \cdot \omega_c}{Q} \right) = 0 \text{ ————— } \textcircled{1}$$

$$\omega_c^2 - \omega_o^2 - \left(\frac{\omega_o \cdot \omega_c}{Q} \right) = 0 \text{ ————— } \textcircled{2}$$

- Solving these equation will give 4 roots (two roots per equation).
- Two of these four roots will be negative which are not physical as $\omega_c > 0$.
- The other two roots are;
 The lower cut-off frequency, ω_l and
 The upper cut-off frequency, ω_u .

$$\omega_l = \omega_o \sqrt{1 + \frac{1}{4Q^2}} - \frac{\omega_o}{2Q}$$

$$\omega_u = \omega_o \sqrt{1 + \frac{1}{4Q^2}} + \frac{\omega_o}{2Q}$$


Series RLC Band Pass Filter

Using voltage divider formula:

$$H(j\omega) = \frac{V_o}{V_{in}} = \left(\frac{R}{R + X_L + X_C} \right) = \left(\frac{R}{R + j\omega L + \frac{1}{j\omega C}} \right)$$

$$H(j\omega) = \left(\frac{R}{R + j\left(\omega L - \frac{1}{\omega C}\right)} \right)$$

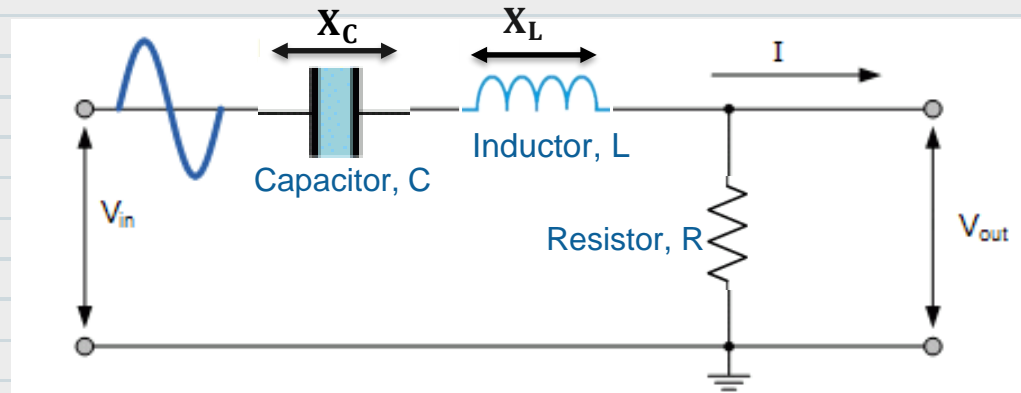- $$H(j\omega) = \left(\frac{1}{1 + j\left(\frac{\omega L}{R} - \frac{1}{R\omega C}\right)} \right)$$



Finding filter parameters: K , ω_o , ω_u , and ω_l ;

Transform the transfer function to a form similar to the general form of the transfer function for second order band pass filters;

$$H(j\omega) = \frac{K}{1 + jQ\left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega}\right)}$$

Considering RLC band pass filter;

$$H(j\omega) = \left(\frac{1}{1 + j\left(\frac{\omega L}{R} - \frac{1}{R\omega C}\right)} \right)$$

Comparing $K = 1$ and

$$\frac{Q\omega}{\omega_o} = \frac{\omega L}{R} \Rightarrow \frac{Q}{\omega_o} = \frac{L}{R} \text{ ————— (1)}$$

$$\frac{Q\omega_o}{\omega} = \frac{1}{R\omega C} \Rightarrow Q\omega_o = \frac{1}{RC} \text{ ————— (2)}$$

Solving;

$$\frac{Q\omega}{\omega_o} = \frac{\omega L}{R} \Rightarrow \frac{Q}{\omega_o} = \frac{L}{R} \text{ ————— } (1)$$

$$\frac{Q\omega_o}{\omega} = \frac{1}{R\omega C} \Rightarrow Q\omega_o = \frac{1}{RC} \text{ ————— } (2)$$

Substituting Q from 2 to 1;

$$\frac{1}{\omega_o} \times \frac{1}{\omega_o RC} = \frac{L}{R} \Rightarrow \omega_o = \frac{1}{\sqrt{LC}}$$

Substituting ω_o to 2;

$$Q\omega_o = \frac{1}{RC} \Rightarrow Q = \frac{\sqrt{LC}}{RC} = \sqrt{\frac{L}{R^2C}}$$

•

Substitute values of Q and ω_o the lower cut-off frequency, ω_l and the upper cut-off frequency, ω_u ;

$$\omega_l = \omega_o \sqrt{1 + \frac{1}{4Q^2}} - \frac{\omega_o}{2Q}$$

$$\omega_u = \omega_o \sqrt{1 + \frac{1}{4Q^2}} + \frac{\omega_o}{2Q}$$

Input impedance of the RLC band pass filter, Z_i ;

$$Z_i = R + j\omega L + \frac{1}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$Z_i|_{\min} = R \quad \text{occurs at} \quad \omega = \omega_0$$

The output impedance of the RLC band pass filter, Z_o ;

$$Z_o = R \parallel \left(j\omega L + \frac{1}{j\omega C}\right) \quad \text{and} \quad Z_o|_{\max} = R$$

•


•

Example:

In a series RLC, circuit $R = 30\ \Omega$, $L = 15\ \text{mH}$, and $C = 51\ \mu\text{F}$. Calculate the

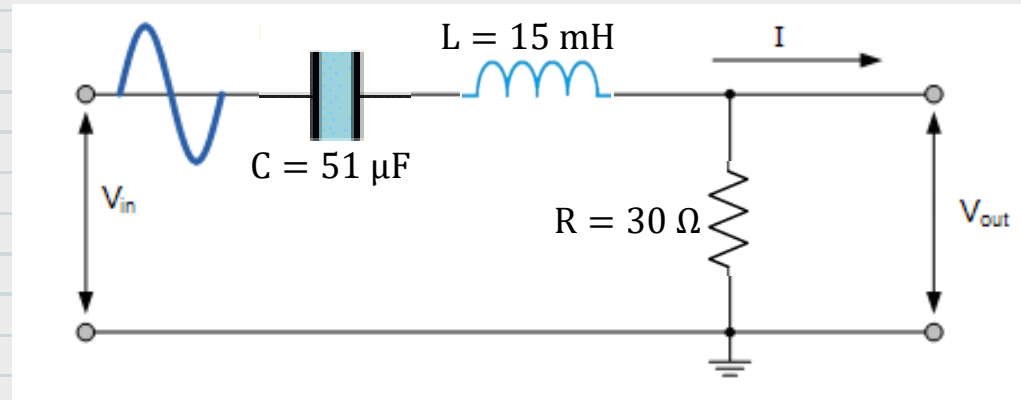- i. Centre frequency, ω_o
- ii. Quality Factor, Q
- iii. Upper cut-off frequency, ω_u
- iv. Lower cut-off frequency, ω_l .

Consider the transformed transfer function of the RLC circuit, to the general form of the transfer function for second order band pass filters, when $K=1$.



Answer:

The general form of the transfer function for second order band pass filters;

$$H(j\omega) = \frac{K}{1 + jQ\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)}$$


$$\text{When } K = 1; \quad H(j\omega) = \frac{1}{1 + jQ\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)}$$

Considering RLC band pass filter;

$$H(j\omega) = \left(\frac{1}{1 + j\left(\frac{\omega L}{R} - \frac{1}{R\omega C}\right)} \right)$$

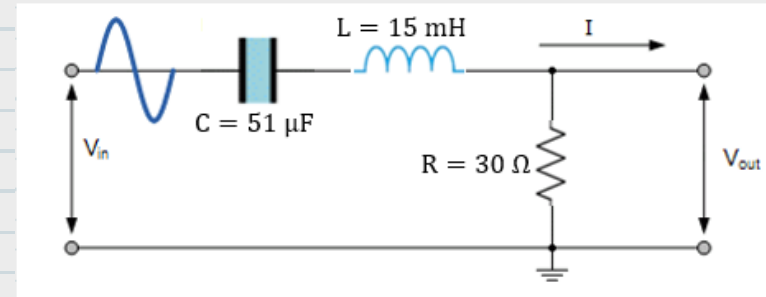i. Calculate center frequency, ω_0

$$\begin{aligned} \omega_0 &= \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{15 \times 10^{-3} \times 51 \times 10^{-6}}} \text{ Hz} \\ &= 8.75 \times 10^4 \text{ Hz} \end{aligned}$$



Answer:

ii. Calculate the quality factor, Q

$$Q = \sqrt{\frac{L}{R^2 C}} = \sqrt{\frac{15 \times 10^{-3}}{(30)^2 \times 51 \times 10^{-6}}} = 0.572$$


iii. Calculate the upper cut-off frequency, ω_u

$$\omega_u = \omega_0 \sqrt{1 + \frac{1}{4Q^2} + \frac{\omega_0}{2Q}}$$

iv. Calculate the upper cut-off frequency, ω_u


- $\omega_l = \omega_0 \sqrt{1 + \frac{1}{4Q^2} - \frac{\omega_0}{2Q}}$

○

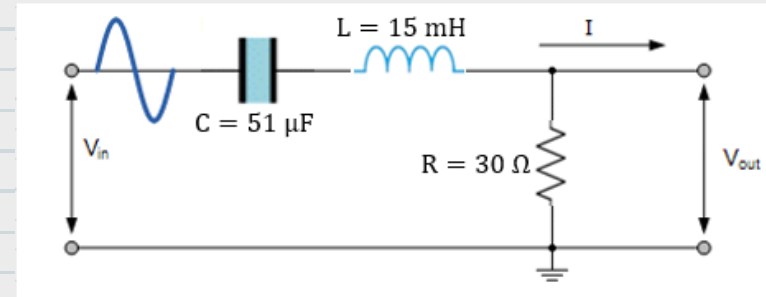


Wide Band Pass Filters

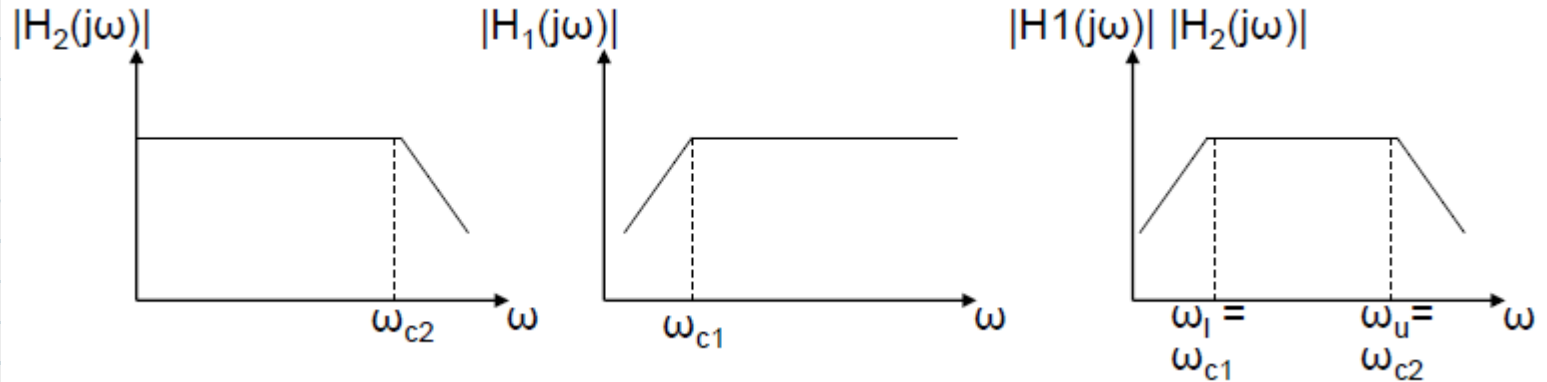- Band-pass filters can be constructed by putting a high-pass and a low-pass filter back to back.
- The high-pass filter sets the lower cut-off frequency and the low-pass filter sets the upper cut-off frequency.



As an Example;

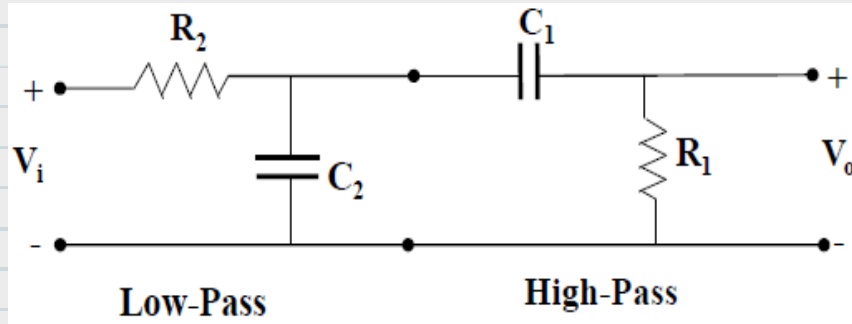

These *RC filters are widely used* (when appropriate) instead of an RLC filter,

Because,

- Inductors are usually bulky
- Can take too much space on a circuit board

¶ In order to have *good voltage coupling*, the input impedance of the high – pass filter, should be much larger than the output impedance of the low-pass filter.

$$Z_{i|_{\min}} = R_1 \gg Z_{o|_{\max}} = R_2$$

or

○

$$R_1 \gg R_2$$

Then, can use un-terminated transfer functions:

$$H(j\omega) = H_1(j\omega) \times H_2(j\omega)$$

$$= \frac{1}{1 + j\frac{\omega}{\omega_{C2}}} \times \frac{1}{1 - j\frac{\omega_{C1}}{\omega}}$$

Where;

$$\omega_{C1} = \frac{1}{R_1 C_1} \quad \text{and} \quad \omega_{C2} = \frac{1}{R_2 C_2}$$

Considering:

$$H(j\omega) = \frac{1}{\left(1 + j\frac{\omega}{\omega_{C2}}\right) \left(1 - j\frac{\omega_{C1}}{\omega}\right)}$$

Can find the filter parameters by transforming the transfer function to a form similar to the general form to give:

$$K = \frac{1}{1 + \frac{\omega_{C1}}{\omega_{C2}}}$$

$$Q = \frac{\sqrt{\frac{\omega_{C1}}{\omega_{C2}}}}{1 + \frac{\omega_{C1}}{\omega_{C2}}}$$

$$\omega_o = \sqrt{\omega_{C1} \cdot \omega_{C2}}$$

These filters work only when $\omega_{C2} \gg \omega_{C1}$, so they are called “*wide-band*” filters.

For these wide-band filters since $\omega_{C2} \gg \omega_{C1}$, can find from above expressions:

$$K = 1 \qquad Q = \sqrt{\frac{\omega_{C1}}{\omega_{C2}}} \qquad \omega_o = \sqrt{\omega_{C1} \cdot \omega_{C2}}$$

$$H(j\omega) = \frac{1}{\left(1 + j\left(\frac{\omega}{\omega_{C2}} - \frac{\omega_{C1}}{\omega}\right)\right)}$$

Then, substitute for Q and ω_o in the expressions for cut-off frequencies to find ω_u and ω_l .

What are the Wide Band and Narrow Band Filters?

Typically, a wide-band filter is defined as a filter with;

$$\omega_{C2} \gg \omega_{C1} \text{ (or } \omega_{C2} \geq 10 \omega_{C1} \text{)}$$

In this case; $Q \leq 0.35$

A narrow-band filter is usually defined as a filter with;

$$B \ll \omega_o \text{ (or } B \leq 0.1 \omega_o \text{)}$$

In this case; $Q \geq 10$

•

•

Resonance


- A **capacitor** presents a **large impedance** to **low frequency ac current**,
But, has a **small impedance** at **high frequency**.
- An **inductor** presents a **large impedance** to **high frequency ac current**,
But, has a **small impedance** at **low frequency**.

Resonance

- A capacitor presents a large impedance to low frequency ac current,
But, has a small impedance at high frequency.
- An inductor presents a large impedance to high frequency ac current,
But, has a small impedance at low frequency.

Consider the series circuit with a capacitor and an inductor connected across an AC generator;

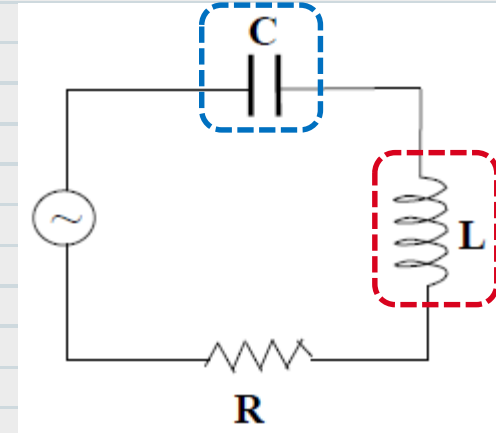- The **impedance** is now large **both** at **high frequencies** (because of the inductor) and at **low frequencies** (because of the capacitor).




Resonance

- A capacitor presents a large impedance to low frequency ac current,
But, has a small impedance at high frequency.
- An inductor presents a large impedance to high frequency ac current,
But, has a small impedance at low frequency.

Consider the series circuit with a capacitor and an inductor connected across an AC generator;

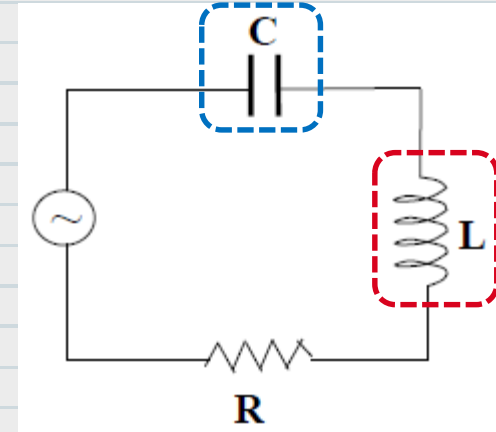- The **impedance** is now large **both** at **high frequencies** (because of the inductor) and at **low frequencies** (because of the capacitor).
- A **minimum** value of **impedance** occurs at **some intermediate frequency** called the **resonance frequency**.



The complex impedance for the circuit;

$$Z = R + j \left(\underbrace{\omega L}_{X_L} - \underbrace{\frac{1}{\omega C}}_{X_C} \right)$$

Magnitude;

$$|Z| = \sqrt{\left[R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2 \right]}$$

It has minimize the impedance (imaginary part) at resonant frequency;

$$Z = R + j \left(\omega L - \frac{1}{\omega C} \right) = 0 \text{ (minimum value)}$$

$$\omega_o L - \frac{1}{\omega_o C} = 0 \quad \Rightarrow \quad \omega_o L = \frac{1}{\omega_o C}$$

$$X_L = X_C$$

Inductive Reactance = Capacitive Reactance

The complex impedance for the circuit;

$$Z = R + j \left(\underbrace{\omega L}_{X_L} - \underbrace{\frac{1}{\omega C}}_{X_C} \right)$$

Magnitude;

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}$$

It has minimize the impedance (imaginary part) at resonant frequency;


$$Z = R + j \left(\omega L - \frac{1}{\omega C} \right)$$

At resonant frequency ω_o given by;


$$\omega_o L = \frac{1}{\omega_o C} \quad \Rightarrow \quad \omega_o = \frac{1}{\sqrt{LC}}$$

The impedance at the resonance is real, having the value of R.

Frequency response of $|Z|$

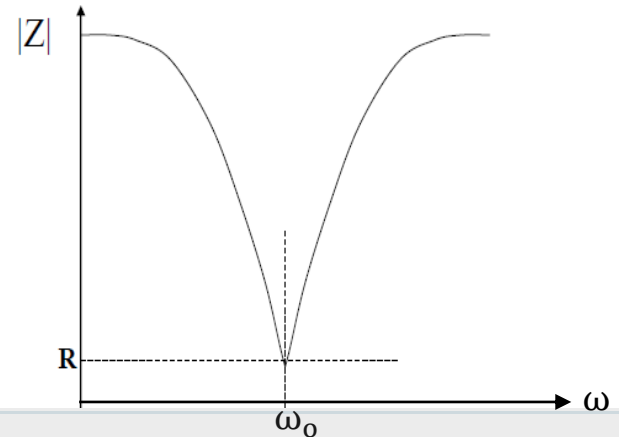

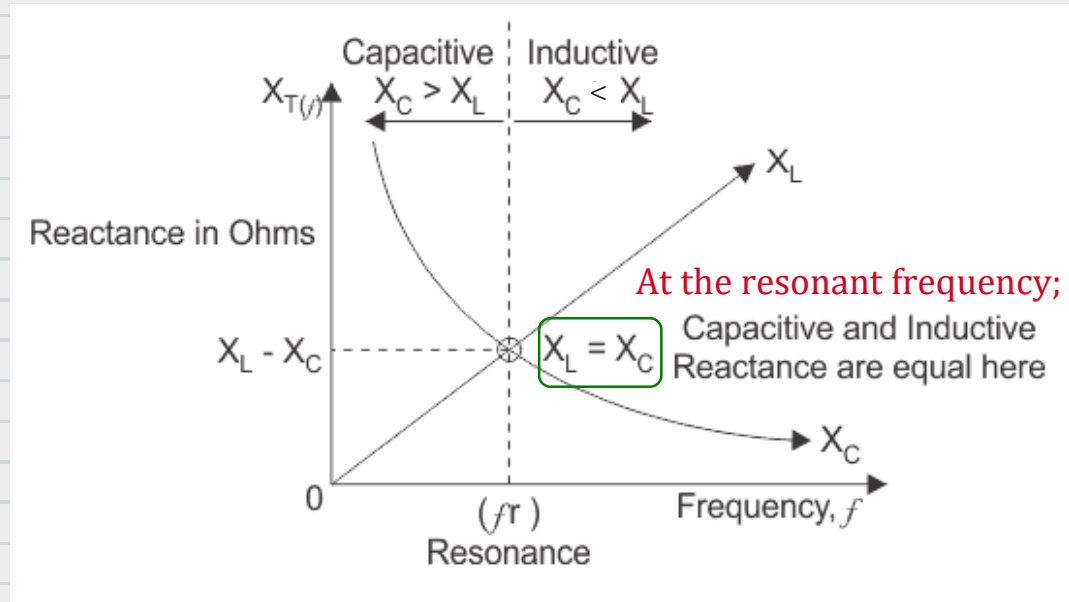
- If the **resistance** of the **inductor** is **very low**,
The **impedance** increases rapidly on either side of the minimum,
as the frequency moves away from the resonant frequency.



- If the resistance of the inductor is very low,
The impedance increases rapidly on either side of the minimum,
as the frequency moves away from the resonant frequency.
- A inductor (coil) and capacitor connected in series can thus **select signals near their resonant frequency** and **reject signals of other frequencies** for which the **impedance** is **high**.
- The circuit is then said to be **tuned** to the **resonant frequency**.


Two port network representation

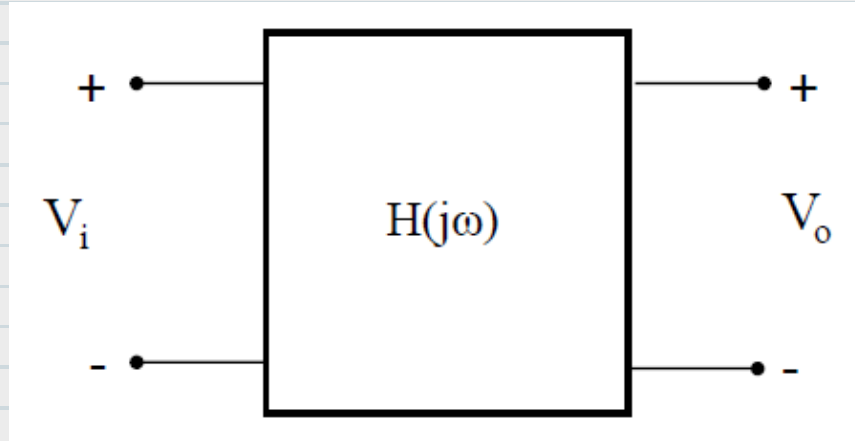- The transfer function characterizes a two port network.



$$H(j\omega) = \frac{V_o}{V_{in}}$$

Bode Plots and Decibels

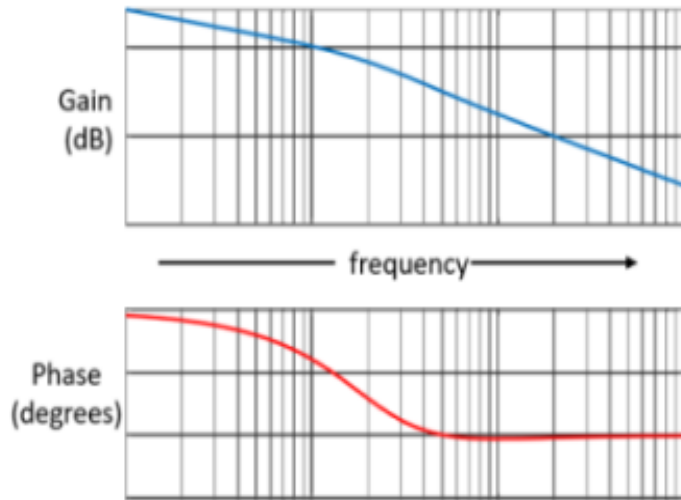

Bode plots show the frequency response, that is, the changes in magnitude and phase as a function of frequency.

This is done on two semi-log scale plots. The top plot is typically magnitude or “gain” in dB. The bottom plot is phase, most commonly in degrees.

Code Plots and Decibels

- The voltage transfer function of a two-port network is usually expressed in Bels:

$$\text{Number of Bels} = \log_{10} \frac{P_O}{P_i} \quad \text{or} \quad = 2 \log_{10} \frac{V_O}{V_i} \quad \left[\because P = \frac{V^2}{R} \text{ and } \therefore P \propto V^2 \right]$$

- But, usually use decibels (dB);

$$\text{Number of decibels} = 20 \log_{10} \left| \frac{V_O}{V_i} \right| \quad \text{or} \quad \left| \frac{V_O}{V_i} \right|_{\text{dB}} = 20 \log_{10} \left| \frac{V_O}{V_i} \right|$$

- Historically, the analog systems were developed first for audio equipment.
- The human ear was constructed to hear both very quiet and very loud sounds of very small and very large frequencies. Therefore the *human ear hears logarithmically*.

- If several two-port networks are placed in a cascade (output of one is attached to the input of the next);

The overall transfer function, ***H***, is equal to the ***product of all transfer functions***.

$$|H(j\omega)| = |H_1(j\omega)| \times |H_2(j\omega)| \times \dots$$

$$20 \log_{10}|H(j\omega)| = 20 \log_{10}|H_1(j\omega)| + 20 \log_{10}|H_2(j\omega)| + \dots$$

$$|H(j\omega)|_{\text{dB}} = |H_1(j\omega)|_{\text{dB}} + |H_2(j\omega)|_{\text{dB}} + \dots$$

... makes it easier to find the overall response of the system.

.

○

◦

◦

THANK YOU!